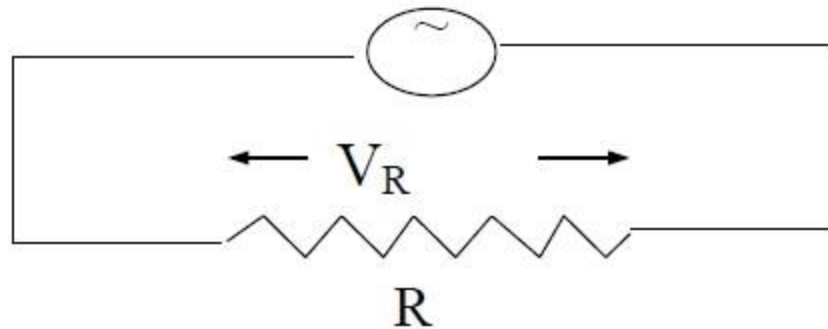


# **Alternating current Circuit Theory**

## AC Circuit with Resistor

consider a circuit containing a resistor  $R$  and source of alternating current (or voltage) as shown in the figure.



Let the current supplies by the A.C. source through the circuit be

$$i = i_o \sin \omega t$$


The instantaneous potential difference  $V_R$  across the resistor is

$$V_R = iR = i_o R \sin \omega t = V_{OR} \sin \omega t$$

Where  $V_{OR} = i_o R$

That the potential difference across the resistor varies sinusoidally and also is in phase with the current.

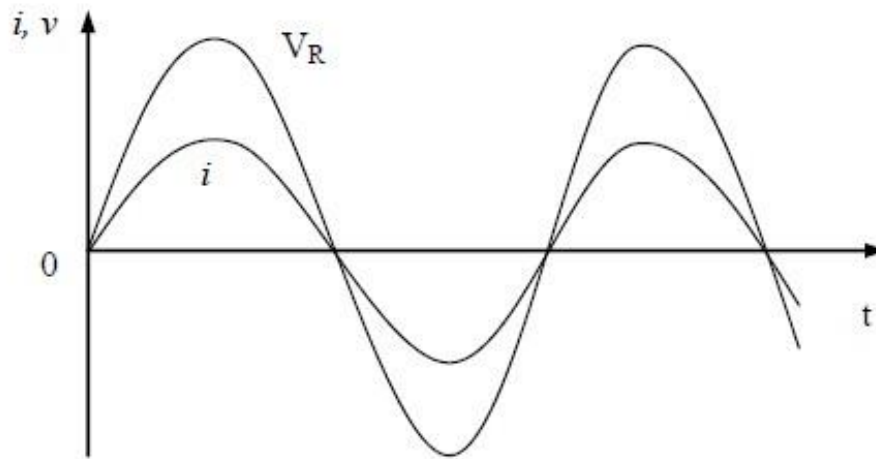That is both  $I$  and  $V_R$  reach their maximum values at the same time as shown in the figure



To find the rms values of the instantaneous voltage,


$$(V_R)_{rms} = R(i_o \sin \omega t)_{rms} = Ri_{rms}$$

Thus, Ohm's law is applicable to the A.C. circuit of the figure.
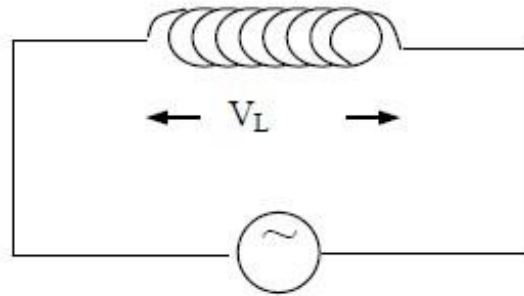
## A.C. Circuit with an Inductor

An AC circuit containing pure inductor is shown in figure.

Even though an inductor always has some resistance, we assume that it is small and may be neglected.



The current through the circuit be  $I_Z = I_o \sin \omega t$

The voltage drop  $V_L$  across the inductor is  $V_L = L \frac{dI_Z}{dt}$ , where  $L$  is the inductance.

$$V_L = L \frac{d}{dt} (I_o \sin \omega t) = LI_o \cos \omega t$$

When  $\cos \omega t = 1$  (ie.  $\omega t = 0$ ),

$V_L$  takes its maximum value.


Let it be  $V_{OL}$

Then  $V_{L(\max)} = LI_o \omega t = V_{OL}$

Therefore  $V_L = V_{OL} \cos \omega t$

$$\cos \omega t = \sin \left( \omega t + \frac{\pi}{2} \right) \qquad V_L = V_{OL} \sin \left( \omega t + \frac{\pi}{2} \right)$$

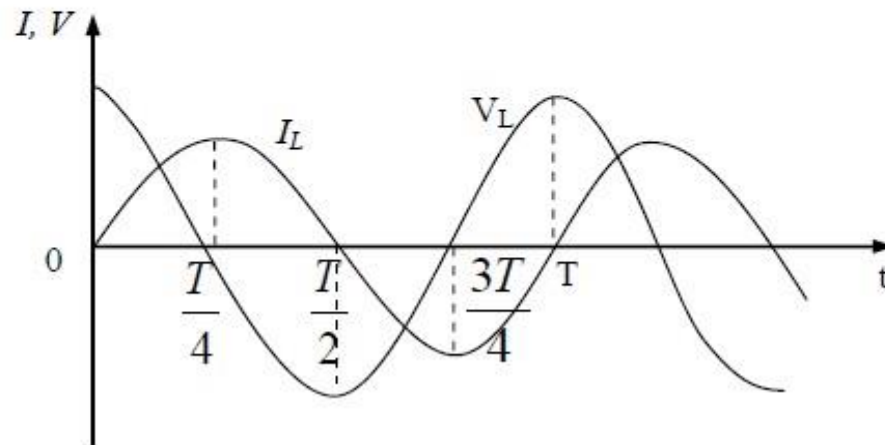The plot of  $V_L$  and  $I_Z$  versus  $t$  is shown in figure.



This indicates that the voltage drop  $V_L$  across the inductor is not in phase with the current.

The voltage drop  $V_L$  across a pure inductor is  $\frac{\pi}{2}$  or  $90^\circ$  or  $\frac{1}{4}$  cycle ahead of the current  $I_Z$ .

This means that when the current  $I_Z$  is zero,  $V_L$  has its maximum value.

Graphs of  $V_L$  and  $I_Z$  versus  $t$  showing that  $V_L$  leads  $I_Z$  by  $\frac{\pi}{2}$ .



Using the equation  $V_L = \omega L i_o \cos \omega t$

The instantaneous value of  $V_L$  can be taken.

$$(V_L)_{rms} = \omega L (i_o \cos \omega t)_{r.m.s}$$

$$(V_L)_{rms} = \omega L i_{rms}$$

Comparing this equation with Ohm's law ( $V = IR$ ).

The quantity  $\omega L$  behaves like a resistance.

This is called the *inductive reactance*  $X_L$ .

Then,  $X_L = \omega L$ , where the units of  $X_L$  are also Ohms.

Then the above equation can be written as:

$$(V_L)_{\text{r.m.s}} = X_L i_{\text{rms}}$$

This is the form of Ohm's law for an inductor in an A.C circuit where  $X_L$  increases with increasing  $L$ .




## AC Circuit with Capacitance

An A.C. circuit containing a capacitor is shown in the figure.

The current  $I_C$  through the circuit at any instant is given by

$$I_C = I_0 \sin \omega t$$

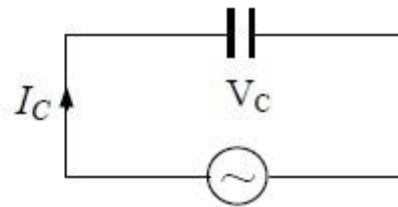

The current entering into the one plate of the capacitor must be equal to the current leaving the other plate.

So that the charges on the two plates are equal and opposite.

The instantaneous voltage  $V_C$  across the capacitor is,

$$V_C = \frac{q}{C} \text{ Where } q \text{ is the instantaneous charge on the capacitor.}$$

To calculate  $V_C$ ,  $q$  must be calculated from  $I_C = I_0 \sin \omega t$

The relation between charge  $q$  and current  $I_C$  is

$$\frac{dq}{dt} = I_C = I_0 \sin \omega t$$

Then  $dq = I_0 \sin \omega t dt$

Integrating  $\int dq = \int I_0 \sin \omega t dt$

$$q = -\frac{I_0}{\omega} \cos \omega t$$

Substituting this value in the above equation  $V_C = \frac{q}{C}$


$$V_C = -\frac{I_o}{\omega C} \cos \omega t$$

$$V_C = -V_{oC} \cos \omega t$$

$$= V_o \sin\left(\omega t - \frac{\pi}{2}\right)$$

Where  $V_{oC} = \left(\frac{I_o}{\omega C}\right) = I_o \left(\frac{1}{\omega C}\right)$

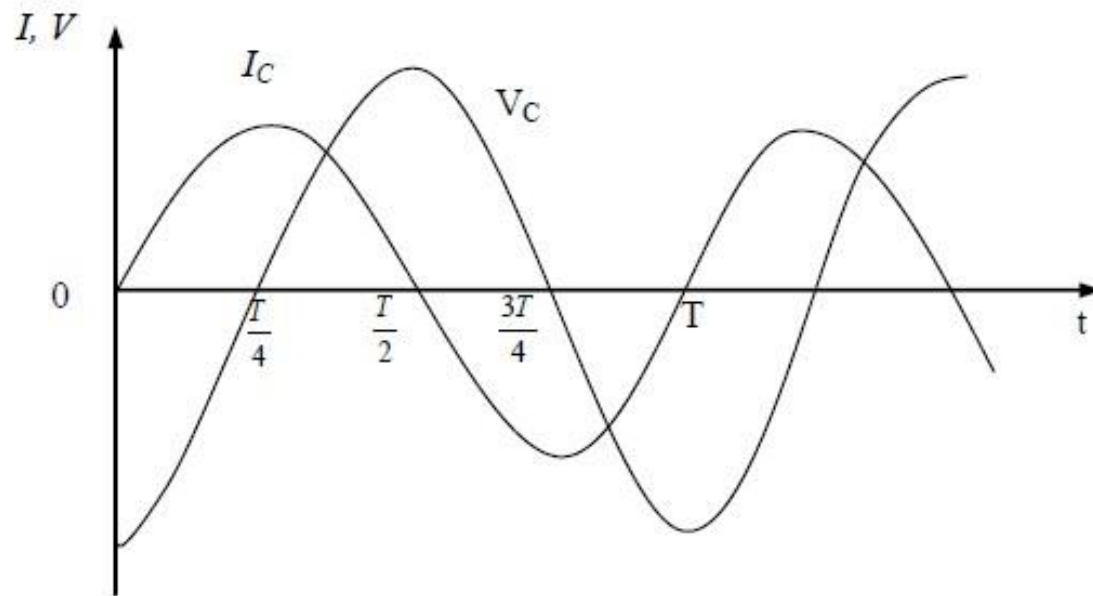The plot of  $I_C$  and  $V_C$  versus  $t$  indicate that the  $V_C$  and  $I_C$  are not in phase (i.e. both  $i$  and  $V_C$  do not reach their maximum value at the same time).



The r.m.s. values

$$V_{C(r.m.s.)} = \frac{1}{\omega C} (-I_o \cos \omega t)_{r.m.s.}$$

$$V_{C(r.m.s.)} = \frac{1}{\omega C} I_{r.m.s.}$$

On comparing this result with Ohm's law, the quantity  $\frac{1}{\omega C}$  is seen to behave like a resistance.

It is called the capacitive reactance  $X_C$ .

$$X_C = \frac{1}{\omega C} \quad \text{where } \omega = 2\pi f$$

$f$ -frequency of the A.C. and unit of  $X_C$  is ohms.

Unlike  $R$ ,  $X_C$  is not constant, it decreases with increasing  $C$ , and  $\omega$ .

Thus for A.C. current of large  $\omega$ , i.e. high frequency, the capacitor is an easy bypass. (i.e. the current goes through it easily) while for  $\omega = 0$ , it has infinite resistance.

Hence no D.C. passes through a capacitor.

## Example:-

Calculate the resistance or the reactance and the voltage across each of the following for an A.C. source with an effective current of 5A and a frequency of 60 Hz, 600 Hz and 6000 Hz for

- (a) resistor of  $10\Omega$ ,
- (b) Inductor of 1H, and
- (c) Capacitor of  $1\mu\text{F}$ . Make plots of  $R$ ,  $X_L$  and  $X_C$  versus  $\omega$ .



## Solution

- (a) The resistance  $R$  is independent of frequency and hence remains constant at  $10\Omega$ . Also  $V_R = IR$  remains constant,

$$V_R = RI = 10\Omega \times 5A = 50V = 50V$$

- (b) From equation  $X_L = \omega L$

Where  $\omega = 2\pi f$  and  $f$  is the frequency

Then  $X_L = 2\pi fL$  and  $V_L = IX_L = 2\pi fLI$

Therefore for,  $f = 60s^{-1}$      $f = 600s^{-1}$      $f = 6000s^{-1}$

$$X_L = 377\Omega \quad X_L = 37770\Omega \quad V_L = 188500V$$

$$V_C = 1885V \quad V_L = 18850V \quad V_L = 188500V$$

(c) From the equation  $X_C = \frac{1}{\omega C}$


$$X_C = \frac{1}{2\pi \times 10^{-6} \text{F} \cdot f}$$

And from equation  $V_C = X_C I = 5X_C$

Therefore, for  $f = 60\text{s}^{-1}$      $f = 600\text{s}^{-1}$      $f = 6000\text{s}^{-1}$

$$X_C = 2650\Omega, \quad 265\Omega, \quad 26.5\Omega$$
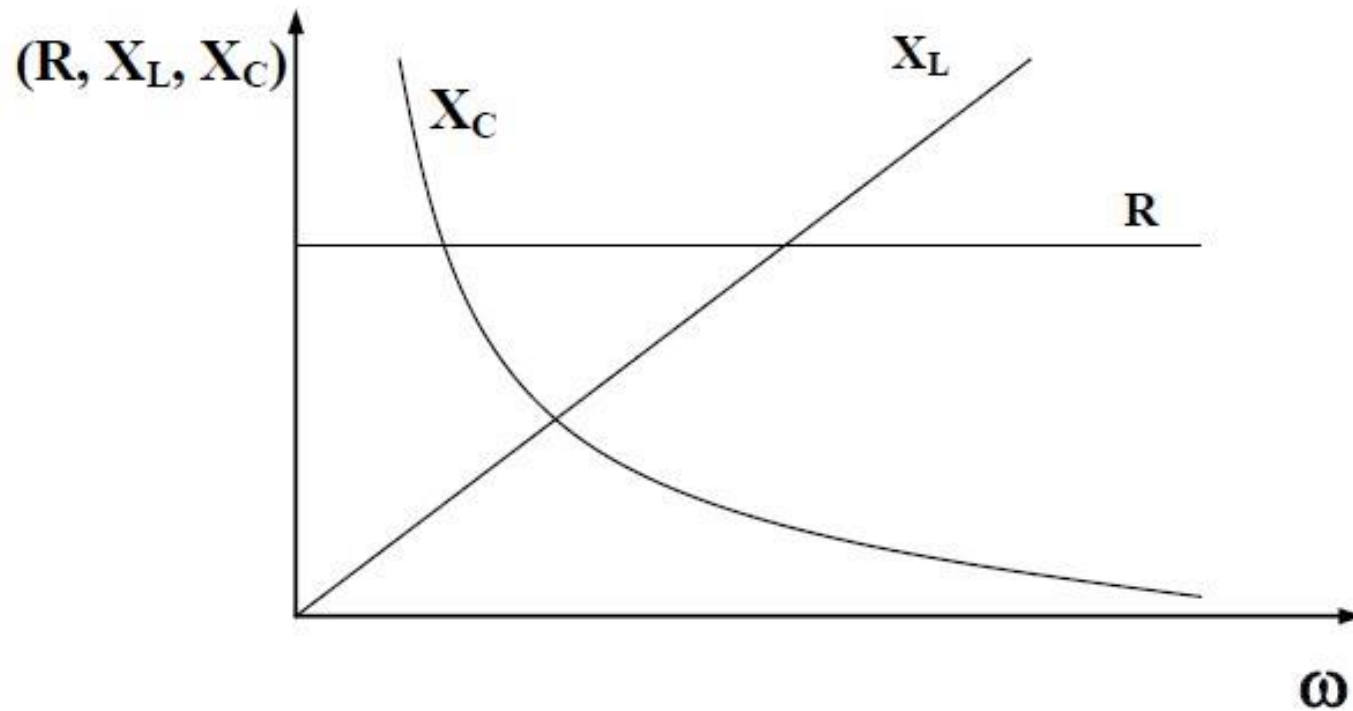
$$V_C = 13250\text{V}, \quad 1325\text{V}, \quad 132.5\text{V}$$




The plots of  $R$ ,  $X_L$  and  $X_C$  versus  $\omega$  are shown in the figure.

Note that  $X_L$  increases with  $\omega$ ,  $X_C$  decreases,  $R$  remains constant.
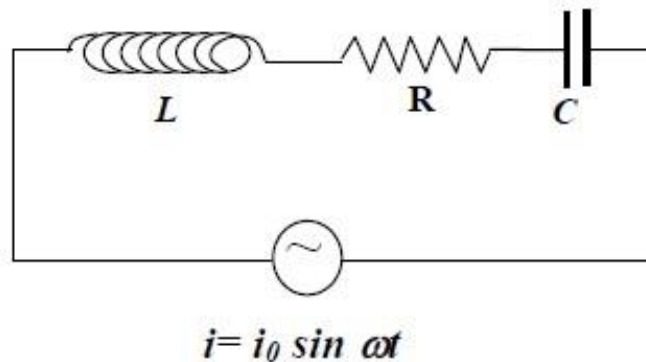
## The L.R.C Series Circuit

A more general case of an AC circuit is the one that contains all three elements, resistance inductance and capacitance as shown in the figure.



Let the instantaneous current  $i$  through any point in the circuit be given

by 
$$I = I_0 \sin \omega t$$

$V_R$ ,  $V_L$  and  $V_C$  are the instantaneous voltages across the resistance, The inductance and the capacitance respectively.

Then, we may write 
$$V = V_R + V_L + V_C$$

Which states that the instantaneous voltage  $V$  across the generator is equal to the sum of the voltages across the elements.


Then 
$$V_R = IR = I_0 R \sin \omega t$$

$$V_L = L \frac{dI}{dt} = I_0 L \omega \cos \omega t = I_0 X_L \cos \omega t$$

where 
$$X_L = \omega L$$

$$V_C = -I_0 X_C \cos \omega t; \text{ where } X_C = \frac{I}{\omega C}$$

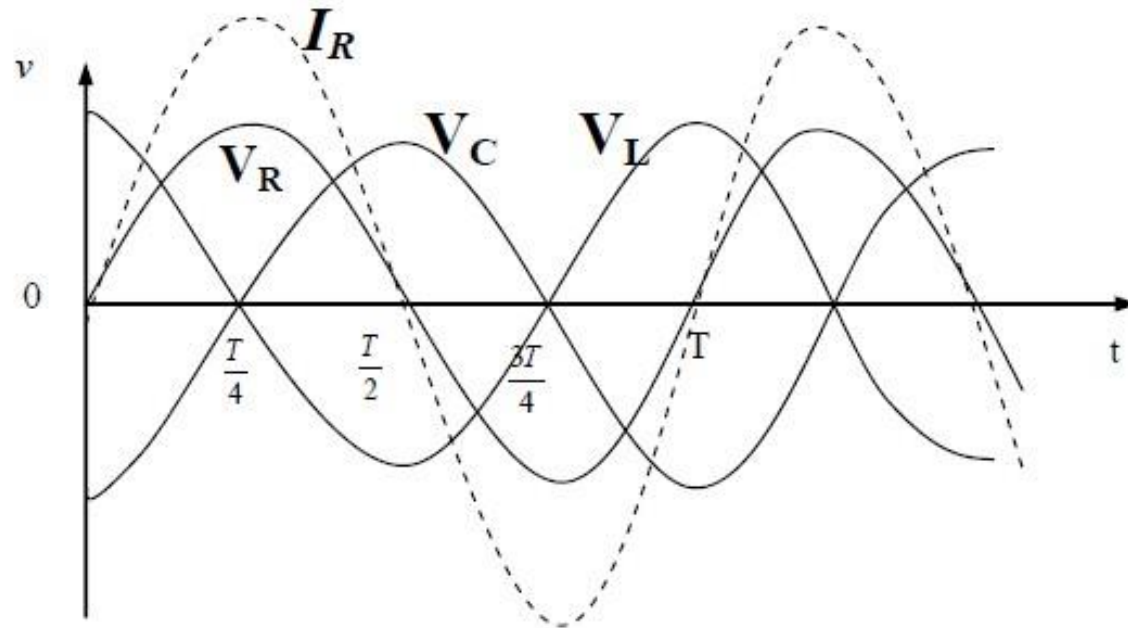The plots of  $V_L, V_R, V_C$ , with  $i$  are shown in the figure



Substituting these values for the voltages.

$$V = I_0 [R \sin \omega t + (X_L - X_C) \cos \omega t]$$



After multiplying and dividing by,  $\sqrt{R^2 + (X_L - X_C)^2}$

$$V = I_0 \sqrt{R^2 + (X_L - X_C)^2} \left( \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}} \sin \omega t + \frac{X_L - X_C}{\sqrt{R^2 + (X_L - X_C)^2}} \cos \omega t \right)$$

Let  $\cos \phi = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$  and  $\sin \phi = \frac{X_L - X_C}{\sqrt{R^2 + (X_L - X_C)^2}}$

Then the above equation takes the form

$$V = I_0 \sqrt{R^2 + (X_L - X_C)^2} \{ \cos \phi \sin \omega t + \sin \phi \cos \omega t \}$$

$$\text{or } V = I_0 \sqrt{R^2 + (X_L - X_C)^2} \{ \sin(\omega t + \phi) \}$$

Where,  $\tan \phi = \frac{X_L - X_C}{R}$

Then equation can be written in the form

$$V = V_o \sin(\omega t + \phi)$$

Where  $V_o = I_0 \sqrt{R^2 + (X_L - X_C)^2}$

If  $\sqrt{R^2 + (X_L - X_C)^2} = Z$

$$V_o = I_o Z$$

with  $X_L = \omega L$  and  $X_C = \frac{1}{\omega C}$

In this general case  $Z$  has taken the place of resistance and it is called the *impedance* of the circuit.

Comparison of equation  $I = I_0 \sin \omega t$  and  $V = V_0 \sin(\omega t + \phi)$  indicates that the voltage  $V$  and current  $i$  are out of phase by an angle  $\phi$ .

The value of  $\phi$  depends on the values of  $X_L$ ,  $X_C$  and  $R$ .

If  $X_L > X_C$ ,  $\tan \phi = \frac{(X_L - X_C)}{R}$  is positive and hence  $\phi$  is positive. **Then the voltage leads the current.**

If  $X_C > X_L$ ,  $\tan \phi = \frac{(X_L - X_C)}{R}$  is negative and hence  $\phi$  is negative. **Then the current leads the voltage.**

# Impedance

The joint effect of resistance and reactance in an AC circuit is known as **impedance**. It is designated by the symbol **Z**.

Impedance is defined as the ratio of the effective voltage to the effective current.

The defining equation is

$$Z = \frac{E_{rms}}{I_{rms}}$$

Impedance is measured in Ohms since  $E_{rms}$  is in Volts and  $I_{rms}$  in Amperes.

(a) For a circuit containing only resistance and inductance, it is clear that,

$$E_o = i_o (R^2 + L^2 \omega^2)^{1/2} = \sqrt{R^2 + X_L^2} i_o$$

Therefore

$$Z = \sqrt{R^2 + X_L^2}$$

Then the current through the circuit is given by,

$$i_o = \frac{E_o}{\sqrt{R^2 + L^2 \omega^2}}$$

(b) For a L-C-R series circuit, as shown above,

$$E_o = i_o \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} = i_o \sqrt{R^2 + (X_L - X_C)^2}$$

Therefore,

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Where  $X_L$  and  $X_C$  are the reactances of L and C respectively.

If X is the net reactance of the circuit  $X = X_L - X_C$

Then the impedance  $Z = \sqrt{R^2 + X^2}$



## Susceptance

The reciprocal value of the reactance is called the *susceptance* and it is denoted by the symbol **B**.

Therefore 
$$B = \frac{1}{X}$$

The unit of susceptance is **Ohm<sup>-1</sup> ( $\Omega^{-1}$ )**

## Admittance

This is defined as the reciprocal of *impedance*. The symbol for admittance is **y**.

$$\text{Thus } y = \frac{1}{Z}$$

The unit of admittance is **Ohm<sup>-1</sup> ( $\Omega^{-1}$ )**

### **Example:-**

A resistor  $R$ , an inductance  $L$  and a capacitor  $C$  are all connected in series with an A.C. supply. The resistance of  $R$  is  $15\Omega$  and for the given frequency the inductive reactance of  $L$  is  $24\Omega$  and capacitive reactance of  $C$  is  $14\Omega$ . If the current in the circuit is  $5A$  find,

- (a) The potential difference across each of the components  $R$ ,  $L$  and  $C$ .

## Solution

$$R = 15\Omega, \quad \omega L = 24\Omega, \quad \frac{1}{\omega C} = 14\Omega, \quad i_o = 5A$$

(i) The potential difference across R is  $V_R = i_o R$

$$V_R = 5 \times 15 = 75V$$

The potential difference across L is  $V_L = i_o L \omega$

$$V_L = i_o L \omega = 5 \times 24 = 120V$$

The potential difference across C is  $V_C = \frac{i_o}{C \omega}$

$$V_C = \frac{i_o}{C \omega} = 5 \times 14 = 70V$$

(ii) The impedance of the circuit is

$$Z = \left[ R^2 + \left( L\omega - \frac{1}{\omega C} \right)^2 \right]^{1/2}$$

$$= [15^2 + (24 - 14)^2]^{1/2}$$

$$= [225 + 100]^{1/2}$$

$$\underline{\underline{Z = 18.02\Omega}}$$

(iii) The voltage of the A.C. supply is obtained as

$$\begin{aligned}V_o &= i_o Z \\ &= 5 \times 325^{1/2} = 5 \times 18.02\end{aligned}$$

$$\underline{\underline{V = 90.138V}}$$

(iv) The phase angle  $\theta$  is given by

$$\tan \theta = \frac{X_L - X_C}{R} = \frac{L\omega - \frac{1}{\omega C}}{R}$$

$$\tan \theta = \frac{24 - 14}{15} = \frac{10}{15}$$

$$\underline{\underline{\theta = 33^\circ 41'}}$$