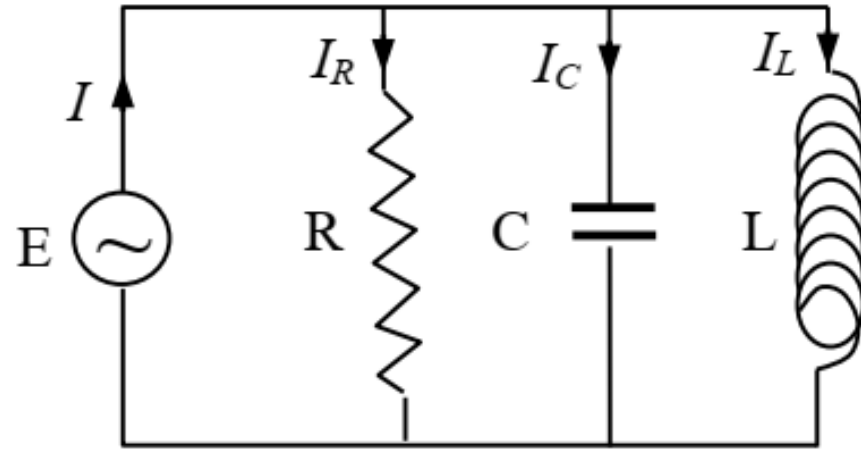


L-C-R Parallel Circuits



Let the branch currents through resistor, capacitor and inductor be I_R , I_C and I_L .


Let $E = E_o \sin \omega t$ be the voltage.

Then, $I = I_R + I_C + I_L$

$$I_R = \frac{E_0 \sin \omega t}{R},$$

$$I_C = C \frac{dv_C}{dt} = C\omega E_0 \sin\left(\omega t + \frac{\pi}{2}\right),$$
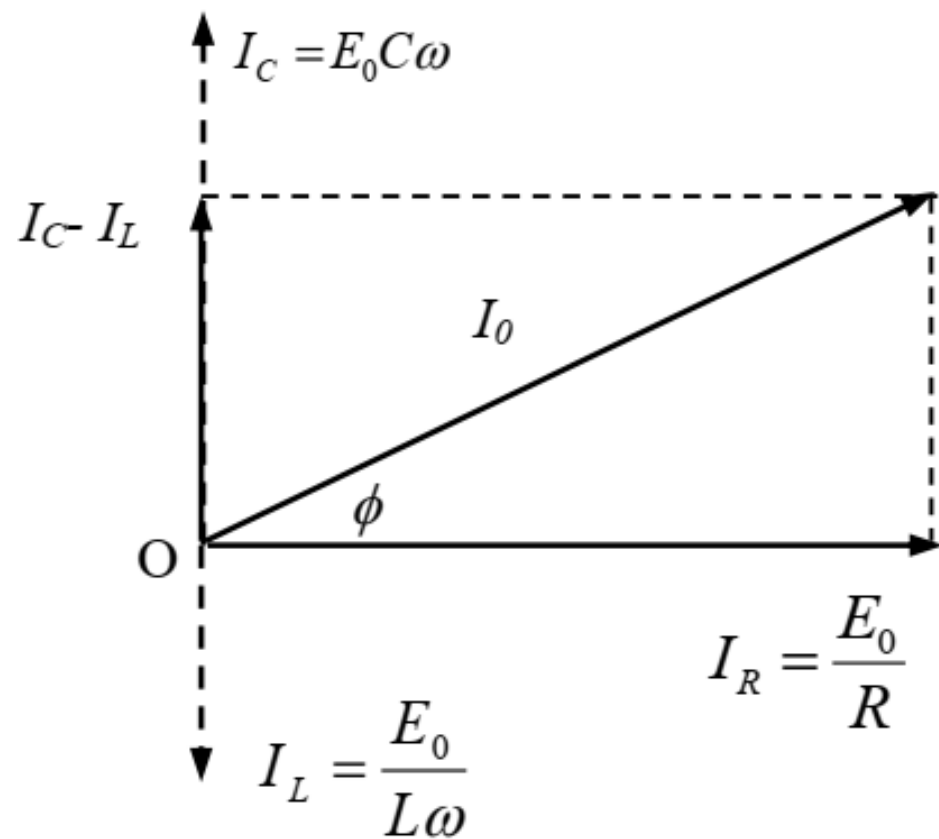
$$I_L = \int \frac{-v_L dt}{L} = \frac{1}{L\omega} E_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$



$$I = \frac{E_0 \sin \omega t}{R} + C\omega E_0 \sin\left(\omega t + \frac{\pi}{2}\right) + \frac{1}{L\omega} E_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$\text{Then, } I_0^2 = \left(\frac{E_0}{R}\right)^2 + E_0^2 \left(C\omega - \frac{1}{L\omega}\right)^2$$

$$I_0 = E_0 \sqrt{\frac{1}{R^2} + \left(C\omega - \frac{1}{L\omega}\right)^2} \quad \text{and} \quad Z = \frac{1}{\sqrt{\frac{1}{R^2} + \left(C\omega - \frac{1}{L\omega}\right)^2}}$$

But $L\omega = X_L$, inductive reactance and $\frac{1}{C\omega} = X_C$, capacitive reactance

Therefore,

$$I_0 = E_0 \sqrt{\frac{1}{R^2} + \left(\frac{1}{X_C} - \frac{1}{X_L} \right)^2}$$

If I makes the angle ϕ with ωt

$$\tan \phi = \frac{C\omega - \frac{1}{L\omega}}{\frac{1}{R}} = \frac{\frac{1}{X_C} - \frac{1}{X_L}}{\frac{1}{R}} = \frac{R(X_L - X_C)}{X_L X_C}$$

Then the current I at any instant can be given by,

$$I = I_0 \sin(\omega t + \phi)$$

The current, therefore leads the potential if $X_L > X_C$ and lags behind if $X_C > X_L$

Resonance

The impedance of a circuit containing inductance resistance, and capacitance connected in parallel is

$$Z = \frac{1}{\sqrt{\frac{1}{R^2} + \left(C\omega - \frac{1}{L\omega}\right)^2}}$$

In this circuit when $\left(C\omega - \frac{1}{L\omega}\right) = 0$ the impedance become it is maximum.

$$\text{Then } L\omega = \frac{1}{\omega C} \quad \text{or} \quad X_L = X_C$$

$$\omega^2 = \frac{1}{LC} \quad \omega = \frac{1}{\sqrt{LC}}$$

Since $\tan \phi = \frac{X_L - X_C}{R}$, phase angle $\phi = 0$, when $X_L = X_C$

Then the current of this circuit is in phase with the voltage which we call the *resonance* condition.

The resonance frequency of the parallel LCR circuit is also $f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$

But when the frequency of the impressed voltage equals this resonance frequency the current in the LCR parallel circuit reaches its minimum.

